



Digital Logic Design and Analysis

December 17

Computer Engineering (Semester 3)

Total marks: 80

Total time: 3 Hours

INSTRUCTIONS

(1) Question 1 is compulsory.

(2) Attempt any **three** from the remaining questions.

(3) Draw neat diagrams wherever necessary.

- 1.a.** Convert $(1762.46)_{10}$ into octal, binary and hexadecimal. (3)
- b.** Prove OR-AND configuration is equivalent to NOR-NOR configuration. (3)
- c.** perform subtraction using 16's complement. (4)
1. $(CB1)_{16} - (971)_{16}$
2. $(426)_{16} - (DBA)_{16}$
- d.** Find 8's complement of following numbers. (2)
1. $(27)_8$
2. $(321)_8$
- e.** Perform the following subtraction $(52)_{10} - (65)_{10}$ using 2's complement method. (2)
- f.** Write the hamming code for 1010. (2)
- g.** Implement the following Boolean equation using NAND gates only.
 $Y = AB + CDE + F$
- h.** Explain the term prime implicant. (2)
- 2.a.** Design a 4-bit ripple adder. (10)
- 3.a.** Implement a full adder using 8:1 multiplexer. (10)
- b.** Implement the following functions using demultiplexer. (5)
- $F_1(A, B, C) = \sum m(0, 3, 7)$ $F_2(A, B, C) = \sum m(1, 2, 5)$
- c.** Simplify $F(A, B, C, D) = \prod M(3, 4, 5, 6, 7, 10, 11, 15)$ and implement using minimum number of gates. (5)
- 4.a.** Compare TTL and CMOS logic with respect to fan in, fan out, propagation delay, power consumption, noise margin, current and voltage parameters. (5)



- b.** Draw the circuit for SR flip-flop using two NOR gates and write the architecture body for the same using structural modelling. (5)
 - c.** Explain 1-digit BCD adder. (5)
- 5.a.** Convert JK flip-flop to SR flip-flop and D flip-flop. (10)
 - b.** Design 3-bit synchronous counter using T flip-flop.
- 6. Write short note on (Any FOUR)**
 - a.** State table (5)
 - b.** ALU IC 74181 (5)
 - c.** Sequence Generator (5)
 - d.** Data flow modelling (5)
 - e.** 4-bit ring counter (5)